

# Phys 330 – Electronics – Lab 6

## Transistors

This is a short 1-week lab. To give you a little break from writing, your report for this lab will be a simple 1 page demonstration that you did the lab. The checklist for what to include is at the end of this document. You may want to read the checklist before starting the lab, so you don't forget things.

## Equipment

- Analog Discovery 2
- Laptop with WaveForms installed
- Breadboard adaptor
- Large breadboard
- Components
  - Transistors: 2N3906, 2N3904, TIP32CG, TIP31CG
  - Resistors: A whole bunch of different values
  - Capacitors: 2x 10  $\mu\text{F}$
  - Jumper wires


## Part 1 – Identifying transistors

First we will do the transistor junction test from last week's homework. Select two transistors from the list in the Equipment section. Do **not** look up their data sheets yet.

For both of the transistors you selected, label the terminals "1," "2," and "3." Using the diode test function of your DMM, complete a table like in problem 3b from homework 7. Using that table, determine the type (npn or pnp) and pinout (which pin is which) for each transistor.

Once you have come up with your answer, check it by looking up the data sheet.

## Part 2 – Emitter follower

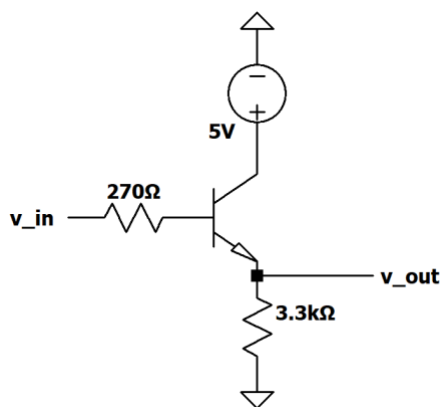

Build the emitter follower circuit shown on the left, using transistor 2N3904. When connecting the transistor, pay close attention to the pinout from the data sheet. I recommend making a small sketch and placing it right on your breadboard to help you keep the pins straight.

Drive  $v_{in}$  with a sine wave of amplitude 3 V. Does  $v_{out}$  look like you predicted in the homework?

Next connect the bottom of the 3.3 k $\Omega$  resistor to -5 V from the V- power supply. Does the output match your prediction from the homework?

We created a circuit with amplification of 1. Can you think of any reason you might want this circuit, instead of just using  $v_{in}$  directly?

## Phys 330 – Electronics – Lab 6

### Transistors

#### Measure input impedance

The base of the transistor draws a small current. We can determine the input impedance by swapping out the base resistor with progressively larger resistors until we see an attenuation from  $v_{in}$  to the base of about 50%. When the attenuation is 50%, we can reasonably conclude that the input impedance is equal to that of the resistor (via the voltage divider equation).

Return the bottom of the 3.3 k $\Omega$  resistor to ground.

Start with a 33 k $\Omega$  resistor instead of the 270  $\Omega$  at the base. How much attenuation do you see? Try larger resistors until you get 50% attenuation. You may want to try using a 100 k $\Omega$  pot (or more) instead – vary the resistance until you get the desired attenuation, then measure the resistance after the fact.

Using the relation,  $Z_{in} = (\beta + 1)Z_{emitter}$ , estimate  $\beta$ .

#### Measure output impedance


Return the 270  $\Omega$  resistor at the base. Measure the peak of the output voltage. This is the “open circuit” voltage for the Thevenin circuit.

Attach a 1 k $\Omega$  “load” from the output to ground. Measure the change in the output voltage.

Using the Thevenin model, you can consider the 1 k $\Omega$  load the lower resistor in a voltage divider, where the upper resistor is the Thevenin impedance, ie the output impedance of the emitter follower. Calculate the output impedance.
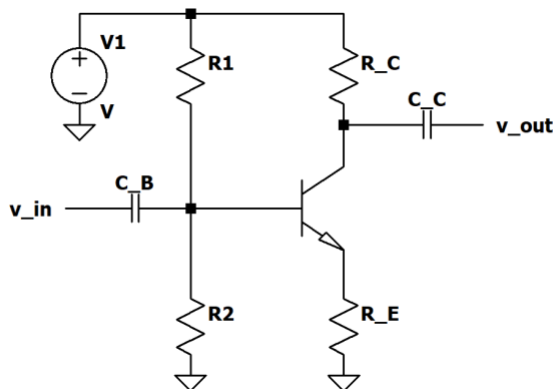
### Part 3 – Common emitter amplifier (optional)

Build the common emitter amplifier we explored in the homework, using transistor 2N3904:



Use the following values:

$V_1 = 5\text{ V}$ ,  $R_1 = 20\text{ k}\Omega$ ,  $R_2 = 10\text{ k}\Omega$ ,  $R_E = 1\text{ k}\Omega$ , and  $R_C = 5\text{ k}\Omega$ , and 10  $\mu\text{F}$  capacitors.

(Note  $V_1$  is different from the homework due to our kit limitations, but you can grab a real power supply if you want.)

Measure the DC operating point (voltages at emitter, collector, and base) and the amplification of the circuit.

Check your measurements using LTSpice (or similar).

## Phys 330 – Electronics – Lab 6

### *Transistors*

## Shortened lab report

Submit a ~1 page report demonstrating you did the lab. Be sure to include the following items:

- Part 1
  - Which transistors did you test?
  - Your diode test table
  - The type and pinout you determined for each transistor
- Part 2
  - A photo of your breadboard setup
  - Your measured input impedance, beta, and output impedance
- Part 3 (optional, 4 points extra credit)
  - A photo of your breadboard setup
  - Your measured DC operating point and amplification
- Your lab notebook as usual